


Basic Electronics

# Electronics

Solderless Breadboard


# Lecture Contents

- How to use a solderless breadboard

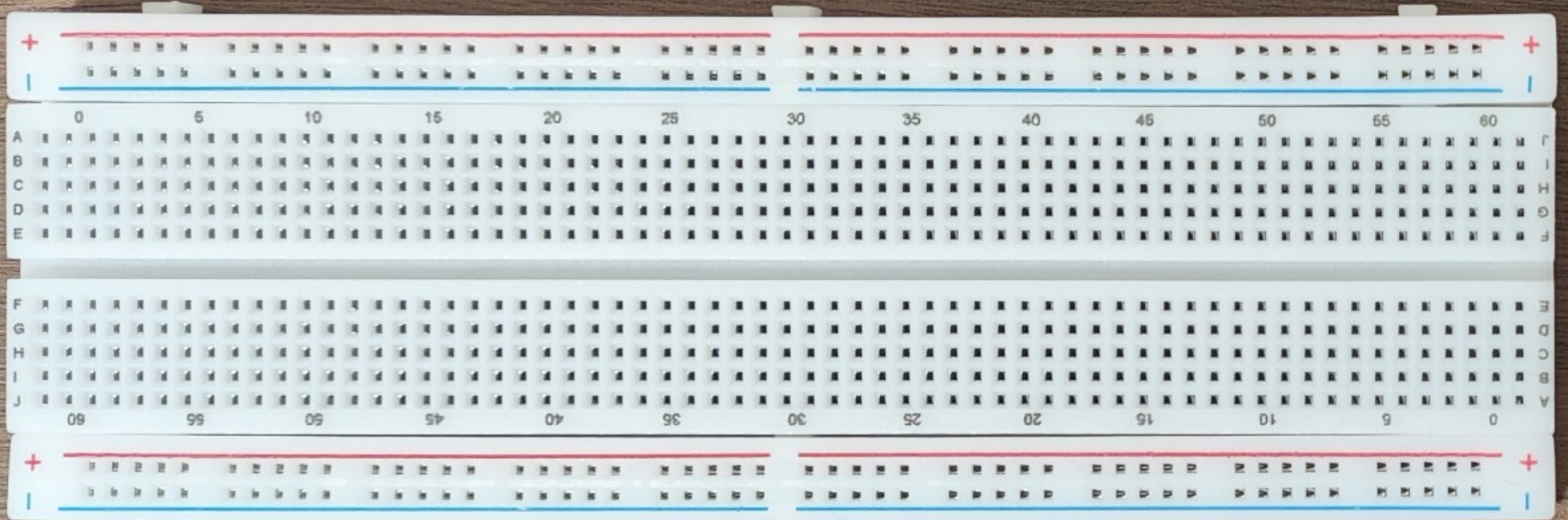

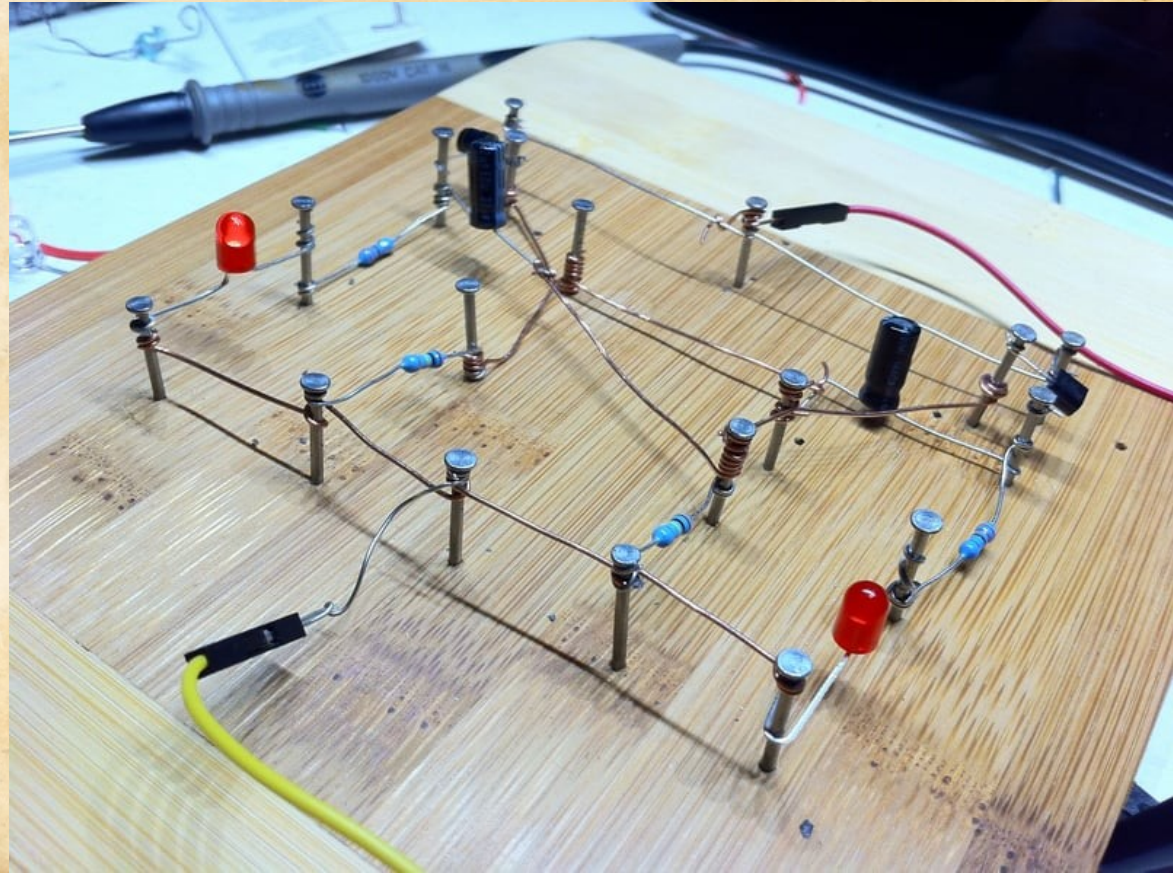
# Why is it a “breadboard”?

- Early electronic hobbyists would literally use wooden breadboards to build their experimental circuits on.




# What is meant by “solderless”?

This is solder


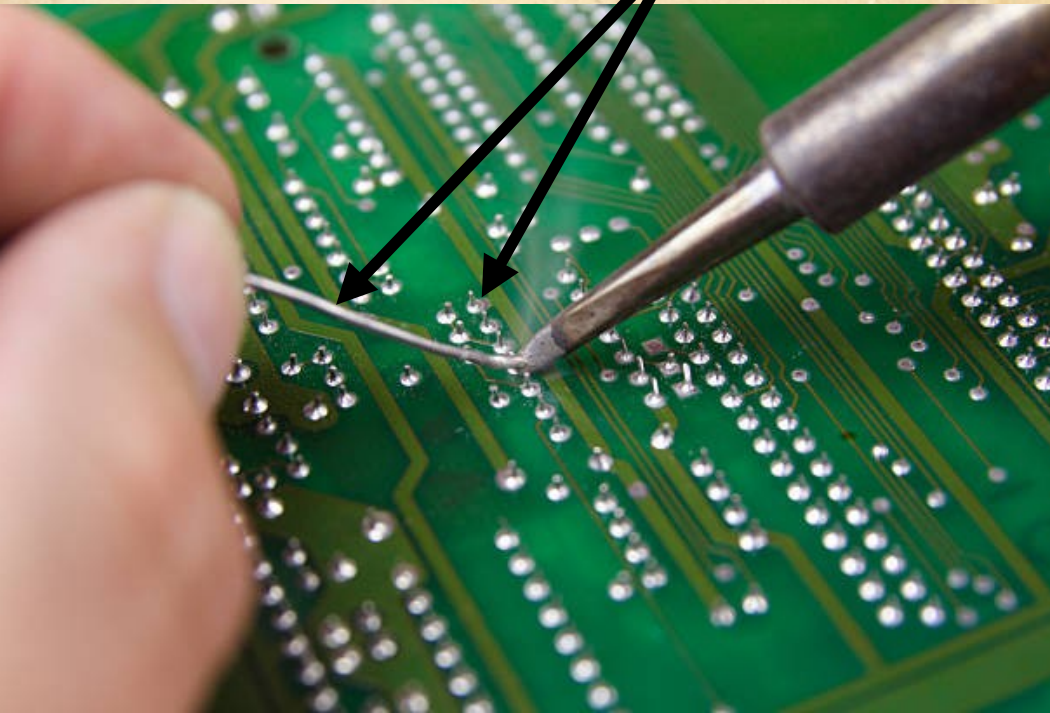


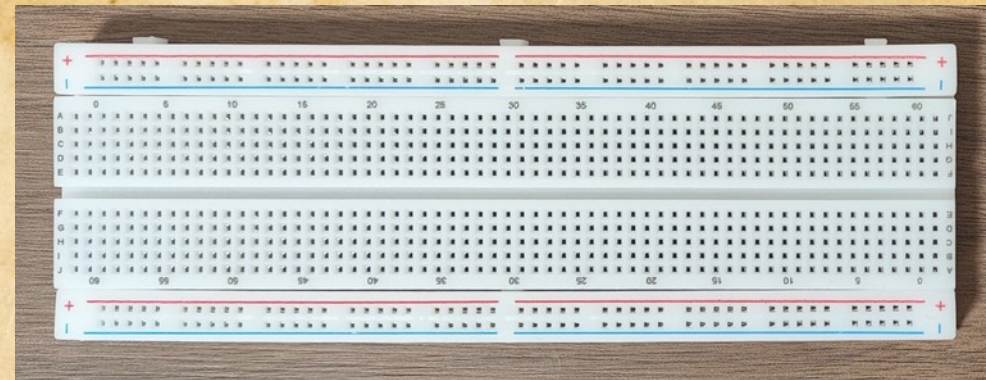We can make connections without solder when using this breadboard.



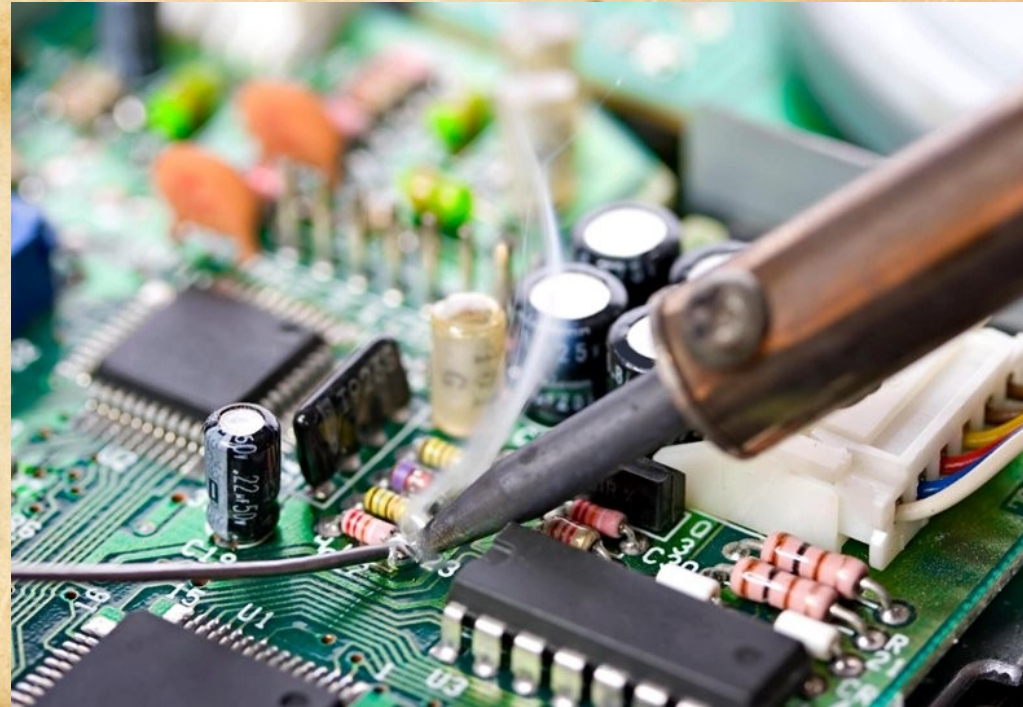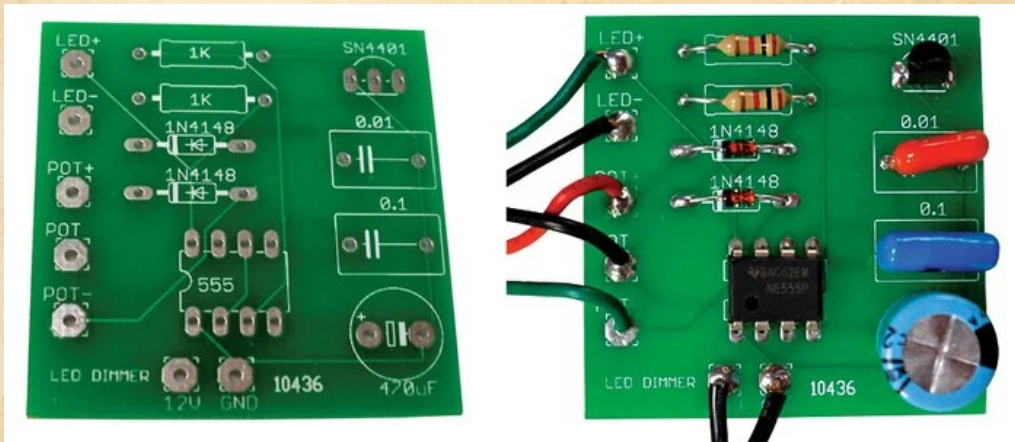
# Printed Circuit Boards (*PCBs*)

- The *breadboard* is used for experimentation and early prototyping.
- For production, a *printed circuit board* is used.



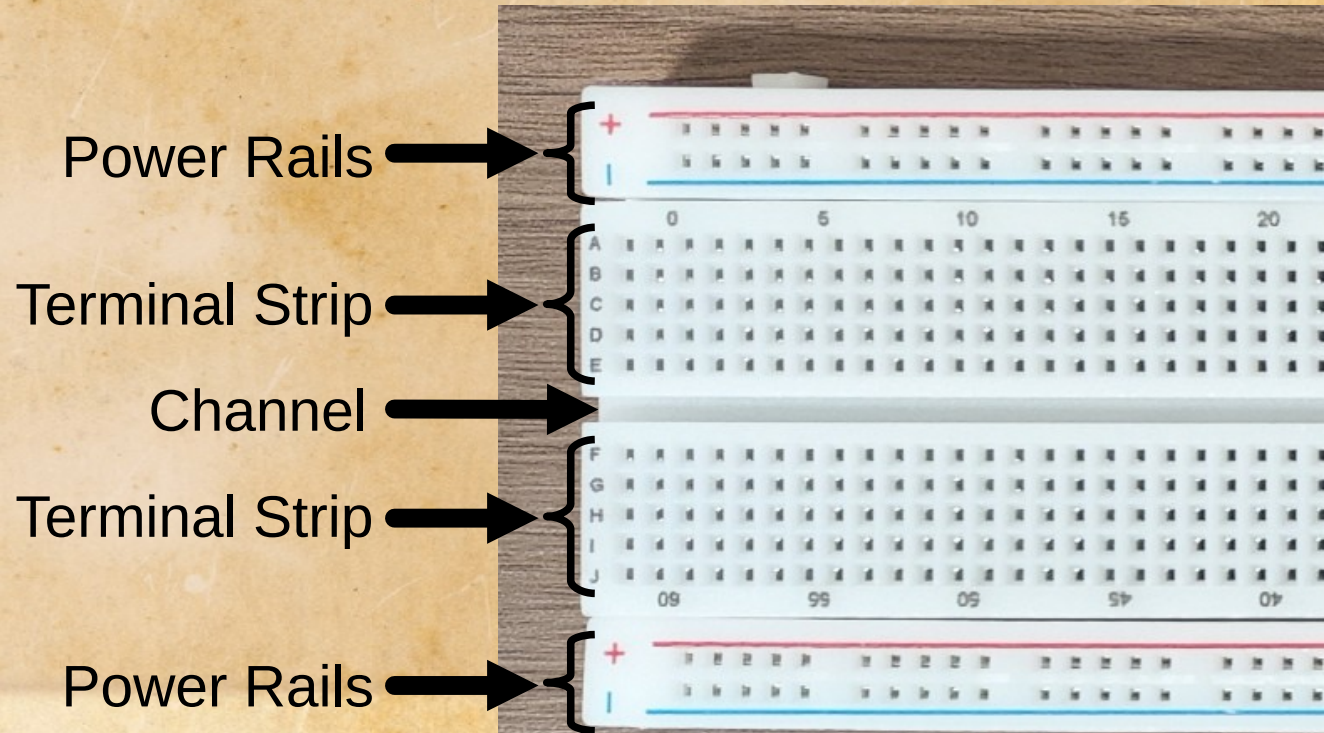
# Parts of a Solderless Breadboard

- In each hole, there is a ***terminal*** containing a spring-loaded conductive grip to provide electrical contact.



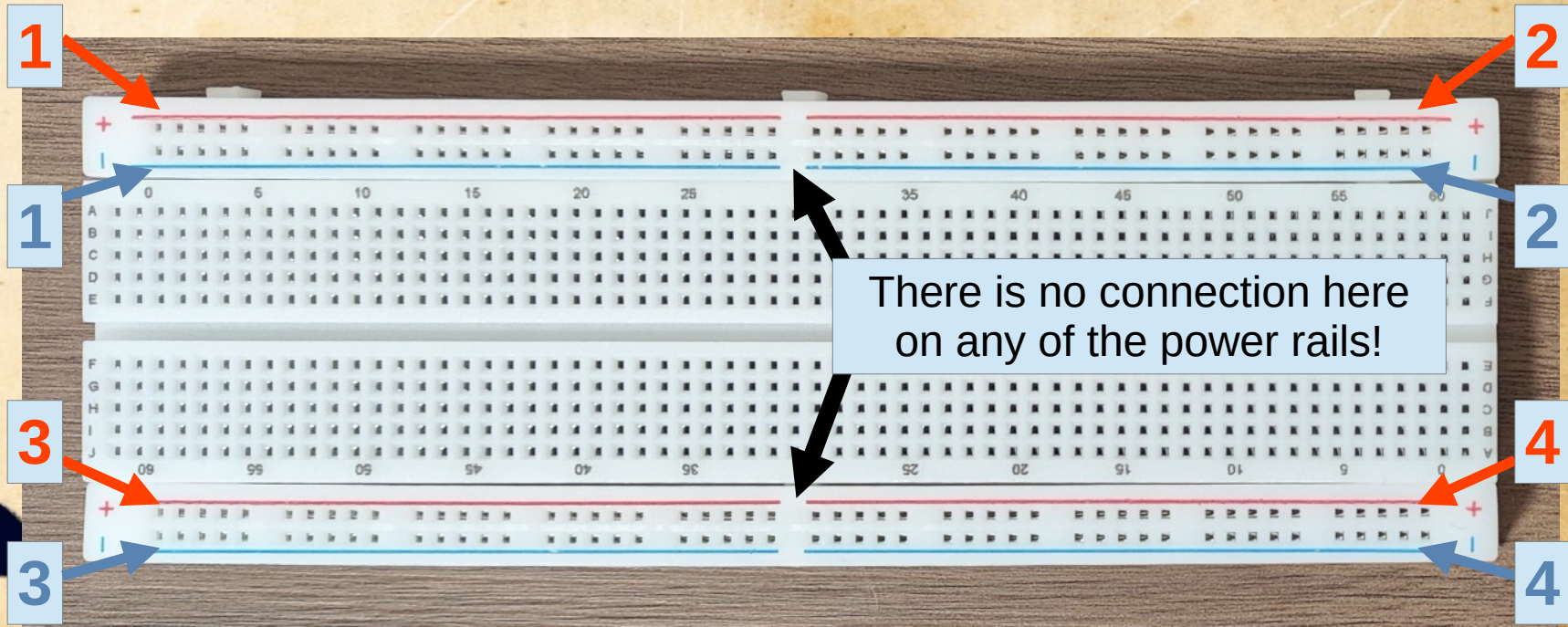
# The Power Rails

- There are 4 separate **positive** and 4 separate **negative power rails**.
  - The holes next to each **red** line are connected, and intended for **positive voltage**
  - The holes next to each **blue** lines are connected, and intended for **negative voltage** (or **ground**).


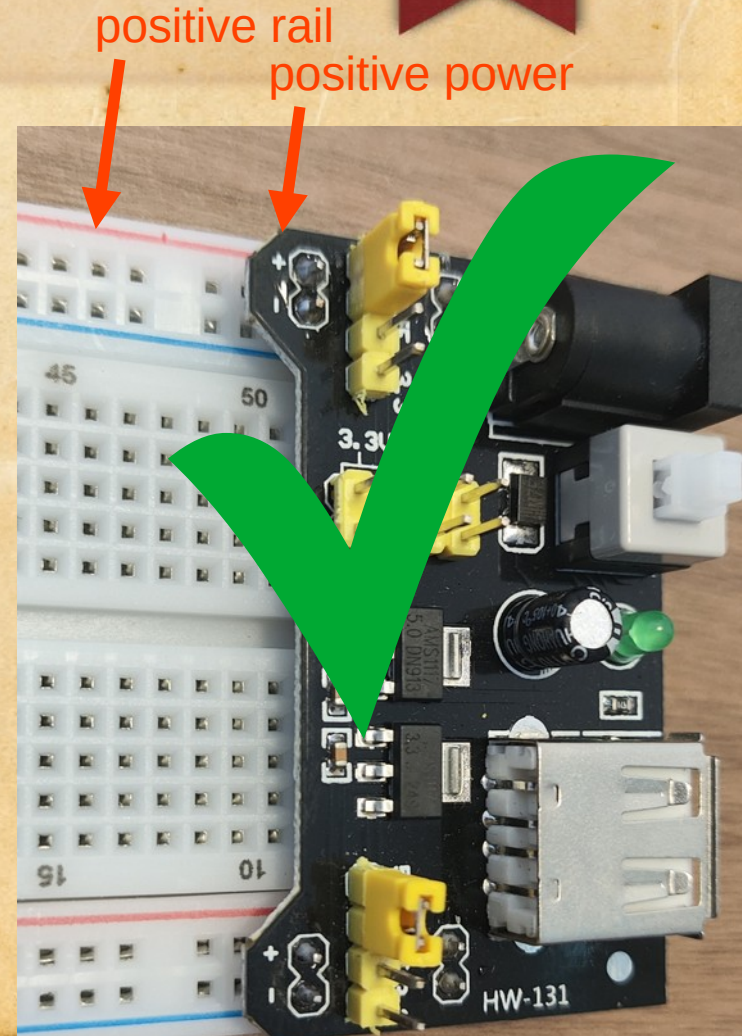
# Inserting the Power Supply


When inserting the power supply, to avoid confusion, ensure the positive power is inserted into the correct (red) power rail.





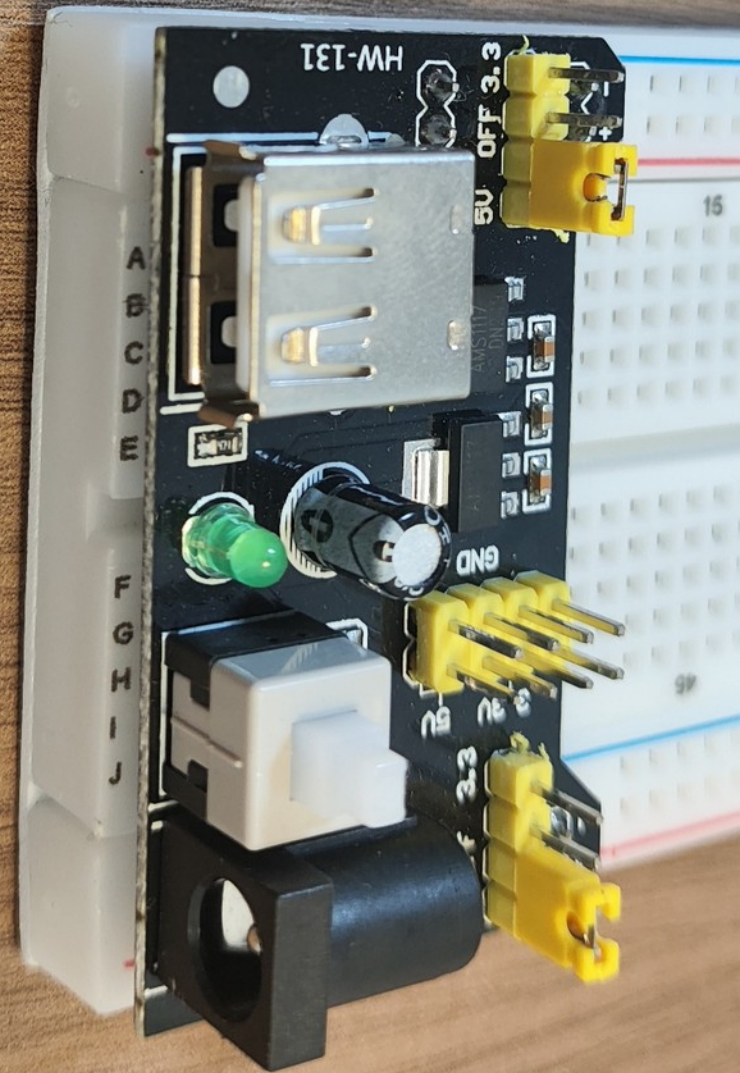
# Connecting the Power Supply

- Align the side of the power supply with the side of the board to prevent damage during storage.
- There shouldn't be a need to remove the power supply during storage.



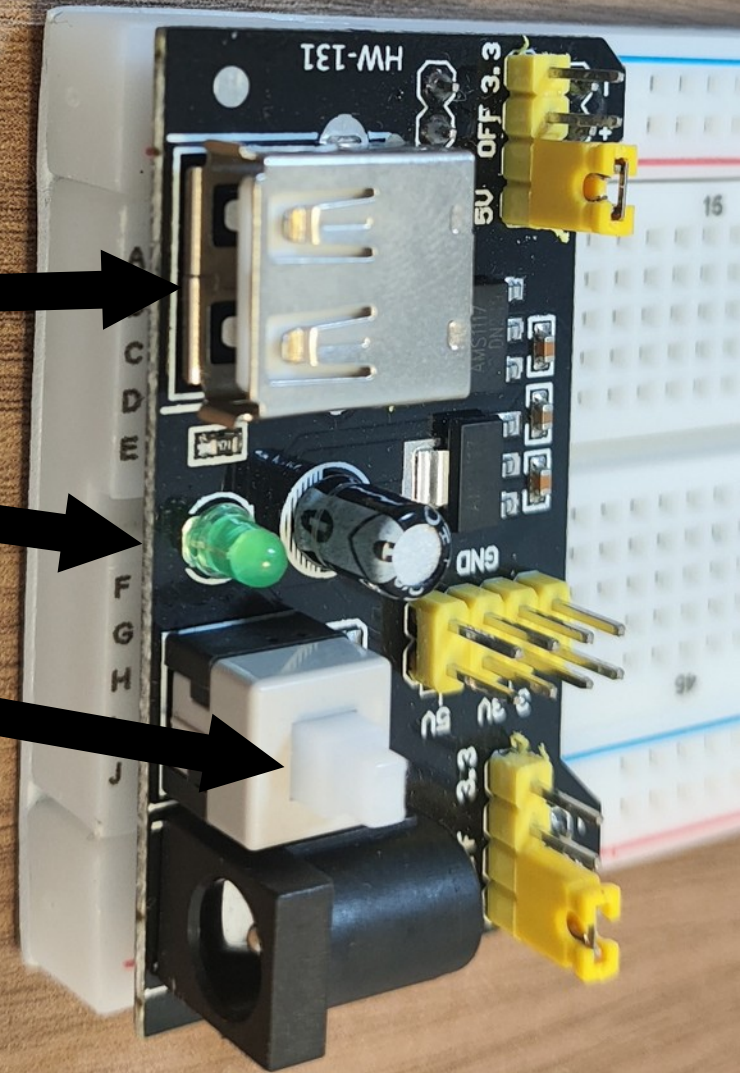
# Connecting the Power Supply

- Connect a USB cable to give power to the power supply.
- The **green LED** will light when the power is turned on.
- This switch toggles the power on and off.



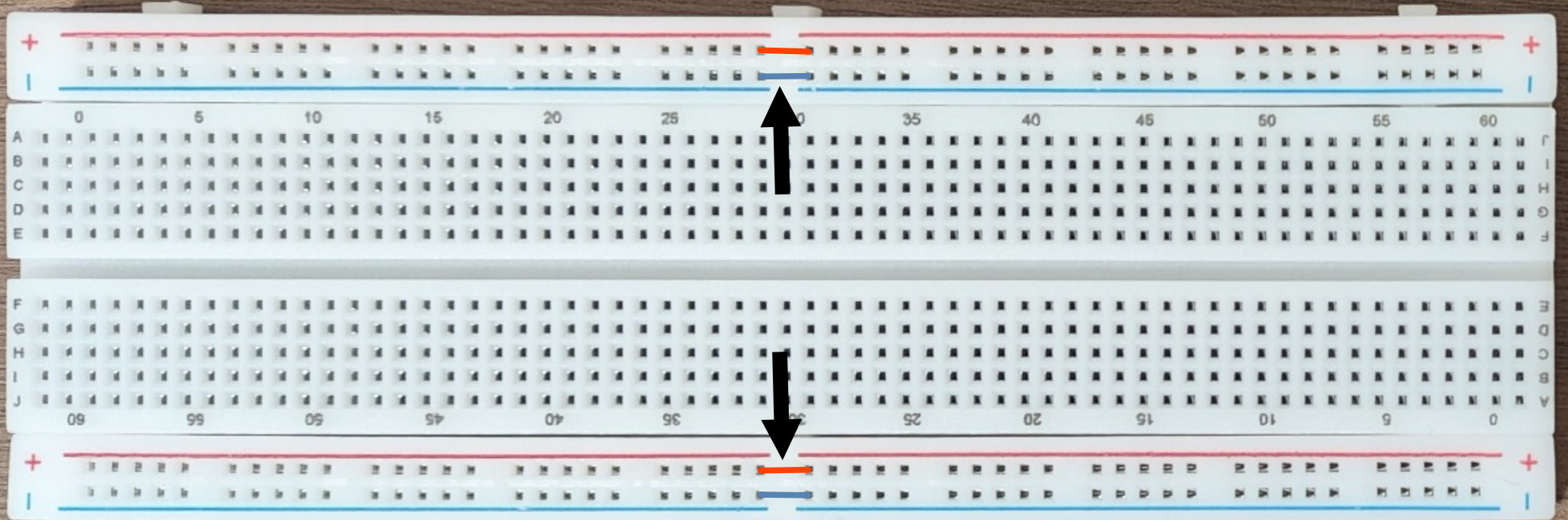
# Lecture Contents

- It may be useful to connect the adjacent power rails with short wires.



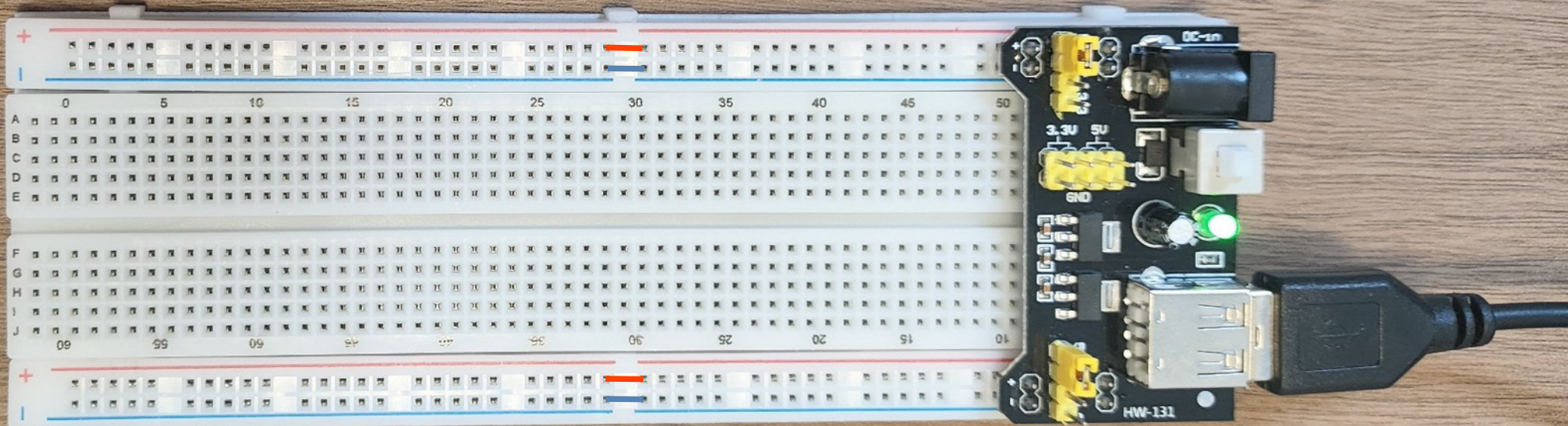
# Powered Breadboard

- This shows the breadboard with the power supply inserted, adjacent power rails connected, and the power turned on.




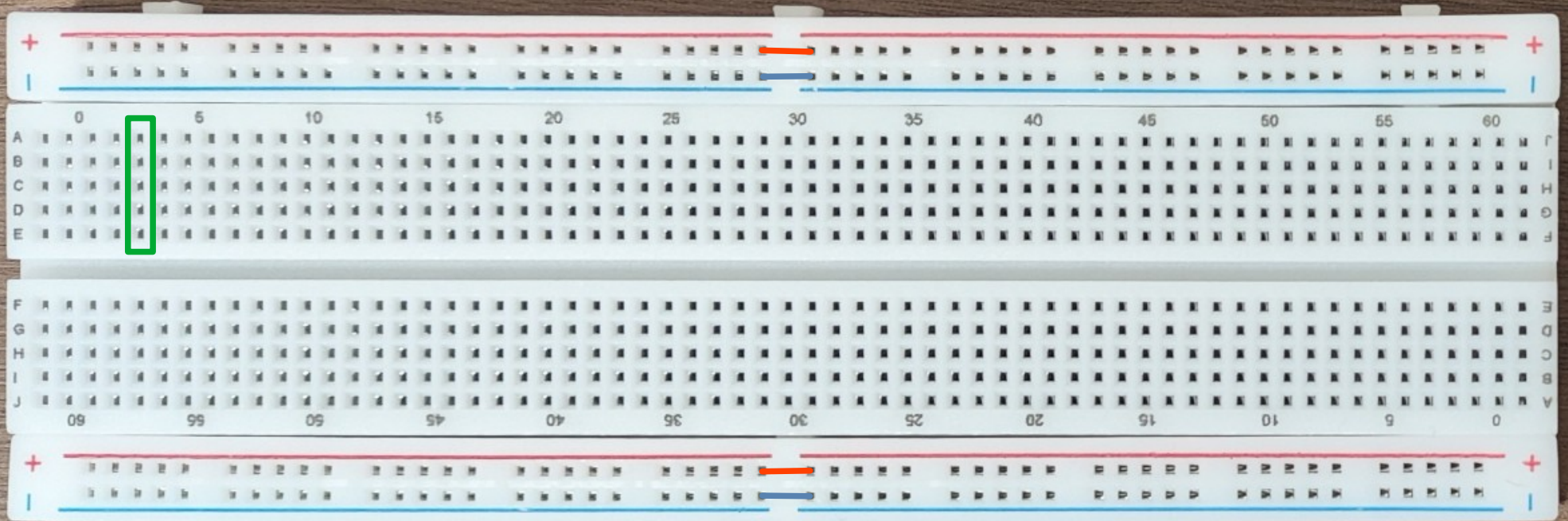
# Terminal Strip Connections

- In the *terminal strip* section, the *terminals* are connected in vertical columns. There is no connection across the center channel.



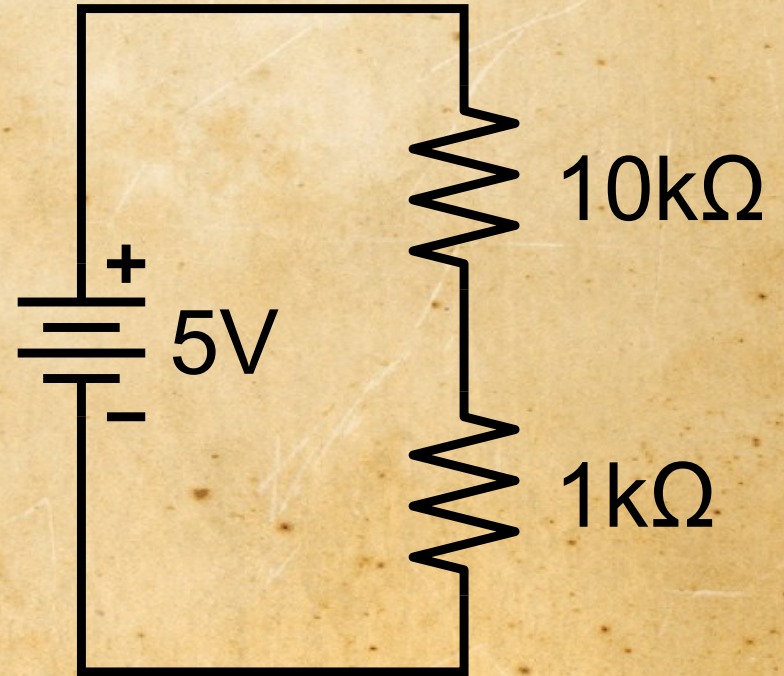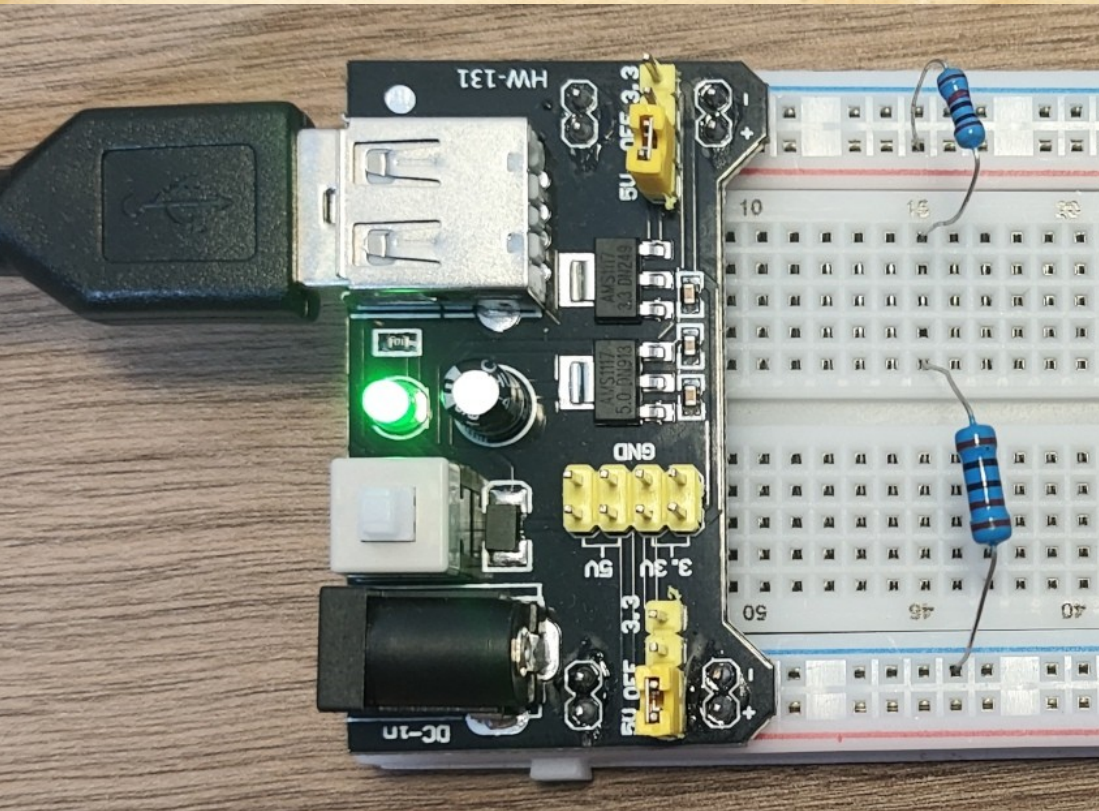
# Example Circuit

- The circuit on the left is an implementation of the diagram on the right.


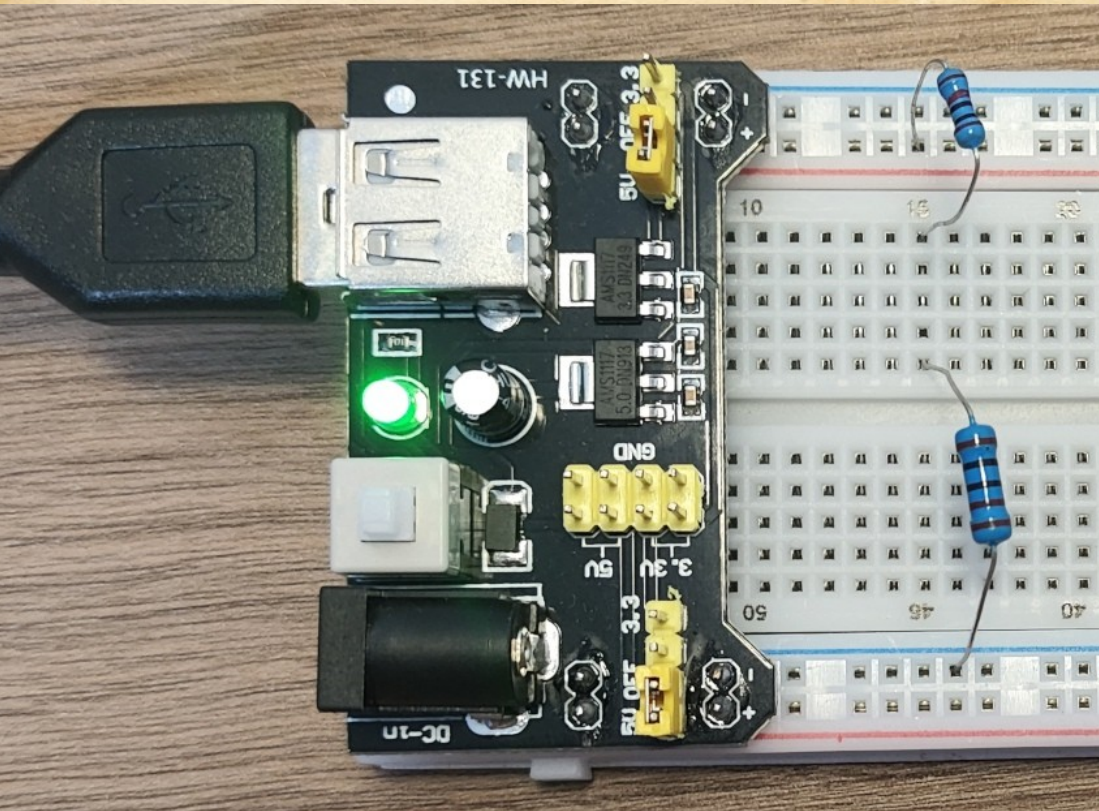
# Example Circuit

- Current is flowing through the circuit created by these connections:



- The power supply is connected to the positive and negative ***power rails***.
- The upper, smaller resistor is connected to the ***positive power rail***.
- The two resistors are connected together using ***column 15***.
- The lower, larger resistor is connected to the ***negative power rail***.

Basic Electronics

# Electronics

Solderless Breadboard